

COMSM1302

Overview of Computer Architecture

Lecture 3

Transistor logic and CMOS



In this lecture

Foundations

- Data representation, logic, Boolean algebra.

Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

Modules

- Memory, simple controllers, FSMs, processors and execution.

Programming

- Machine code, assembly, high-level languages, compilers.



Wrap-up

- Operating systems, energy aware computing.




🔥 The switch - mechanical

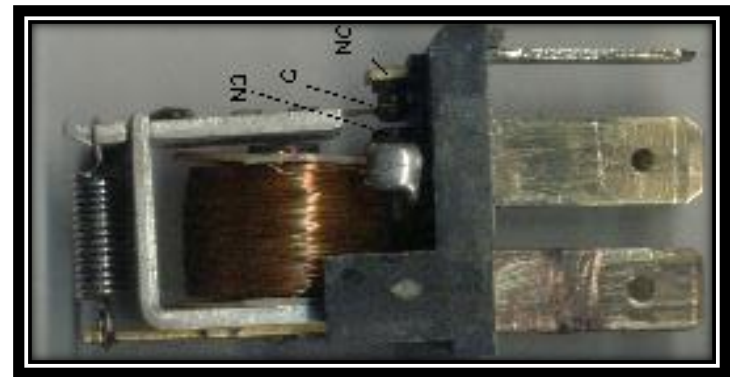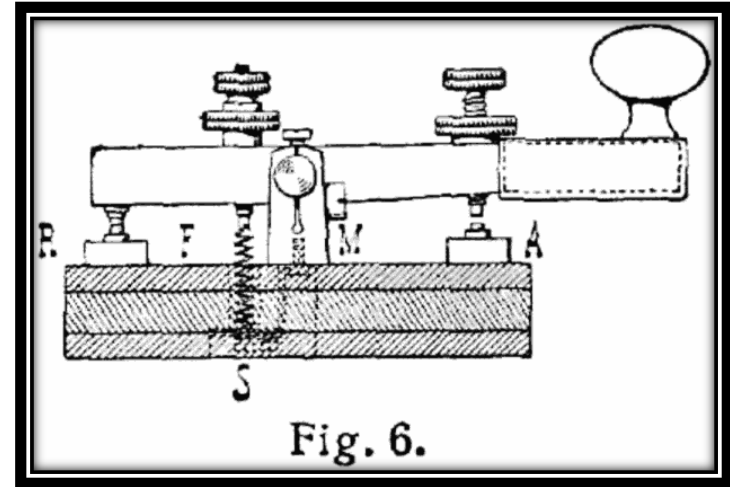- Mechanical switches are very useful
 - Turn things on/off
 - With several switches, we can **encode** more useful things.
- What's wrong with them?



🔥 The switch - valve

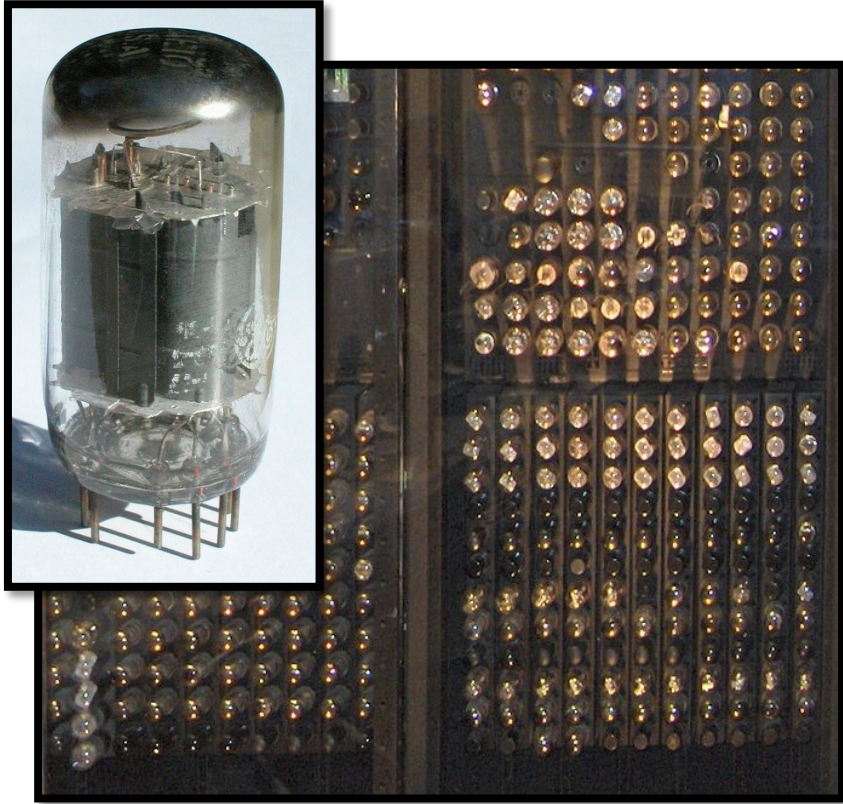

Bank of valves from the ENIAC computer (1946).

Photo [source](#): TexDex, Wikimedia Commons.

- Valves or vacuum tubes.
- Current controlled by **thermionic emission**.
 - They have a **heating element**.
- Quicker than mechanical switches.
- Fairly reliable
 - If they're **kept on!**
 - *ENIAC (1946) used 17,468 vacuum tubes and consumed 150 kW of power.*



The switch - silicon

- Silicon, the element “Si”
 - The second most **abundant element** on Earth.
- A **semiconductor**
 - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.



🔥 The switch – silicon old

- Silicon, the element “Si”
 - The second most **abundant element** on Earth.
- A **semiconductor**
 - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore




🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons

🔥 Wafer

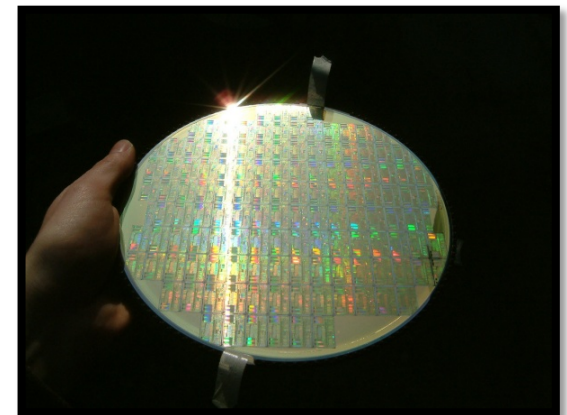

Source: James Irwin, [CC 2.0](#)



The switch - silicon

- Silicon, the element “Si”
 - The second most **abundant element** on Earth.
- A **semiconductor**
 - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

Ore



[Source](#): Stahlkocher, Wikimedia Commons



🔥 The switch - silicon

- Silicon, the element “Si”
 - The second most **abundant element** on Earth.
- A **semiconductor**
 - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore



🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons



🔥 The switch - silicon

- Silicon, the element “Si”
 - The second most **abundant element** on Earth.
- A **semiconductor**
 - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore




🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons

🔥 Wafer

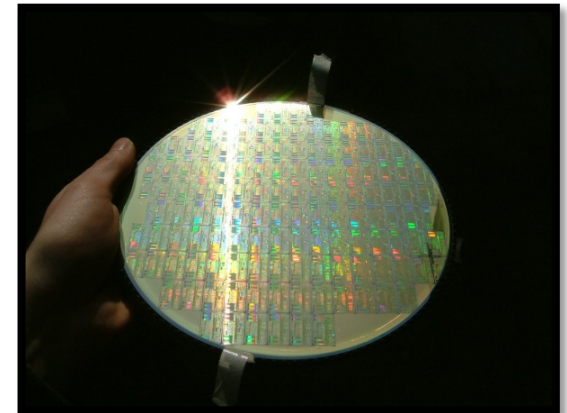


Source: James Irwin, [CC 2.0](#)




🔥 Making a switch out of silicon

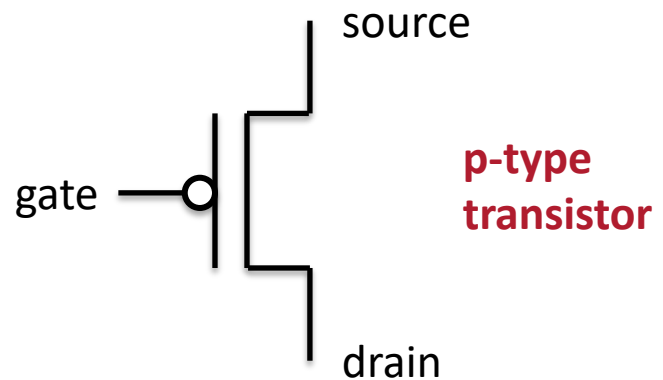- The **transistor**
 - Was invented in 1947 at AT&T's Bell Labs.
- Multiple uses
 - Amplification
 - **Switching**
- Multiple methods of construction
- We are interested in **Integrated Circuits** (ICs), so we want:
Complementary Metal–Oxide–Semiconductor (CMOS) technology.



🔥 Making a switch out of silicon

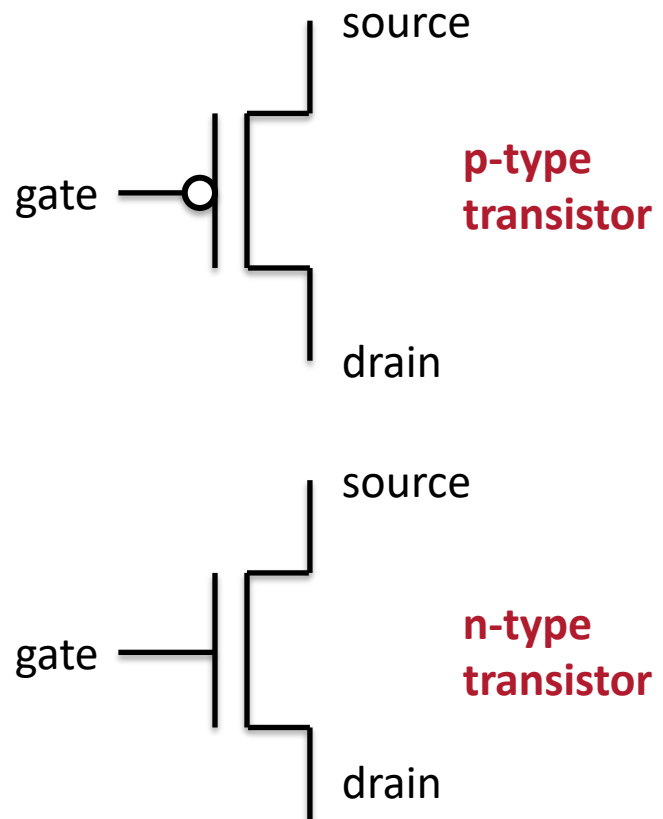
- The **transistor**
 - Was invented in 1947 at AT&T's Bell Labs.
- Multiple uses
 - Amplification
 - **Switching**
- Multiple methods of construction
- We are interested in **Integrated Circuits** (ICs), so we want:
Complementary Metal–Oxide–Semiconductor (CMOS) technology.




n-type and p-type transistors



n-type transistor

 


p-type transistor

 


n-type and p-type transistors



n-type transistor

 


p-type transistor

 


n-type and p-type transistors



n-type transistor

 

p-type transistor


 


🔥 n-type and p-type transistors





n-type transistor

p-type transistor

  

A simple "thought" model:

 
 


🔥 n-type and p-type transistors





n-type transistor

p-type transistor

  


A simple “thought” model:

  


n-type and p-type transistors



n-type transistor

 


p-type transistor

 


n-type and p-type transistors



n-type transistor

 

p-type transistor


 


🔥 n-type and p-type transistors





n-type transistor

p-type transistor

  

A simple “thought” model:

 
 


🔥 n-type and p-type transistors





n-type transistor

p-type transistor

  

A simple "thought" model:

  


🔥 The most basic CMOS circuit

Composition of two complementary transistors


- The power supplies for CMOS are called V_{dd} and V_{ss}
 - V_{dd} = drain supply
 - V_{ss} = source supply
 - “0 V” or “ground” voltage

How does this work?

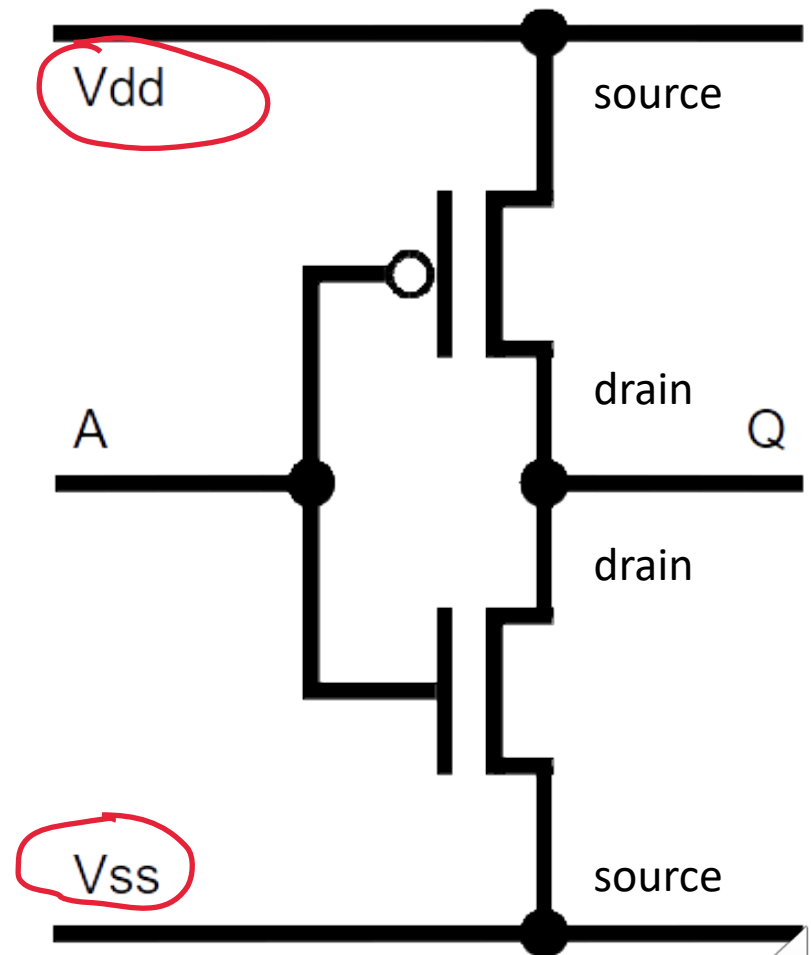


🔥 Modes of operation

 - $A = V_{dd}$.
- The top “switch” is **off/open**.
 - PMOS transistor.
- The bottom “switch” is **on/closed**.
 - NMOS transistor
- Q is “connected” to V_{ss} .



🔥 Modes of operation

 


- $A = V_{ss}$.
- The top “switch” is **on/closed**.
- The bottom “switch” is **off/open**.
- Q is “connected” to V_{dd}.



🔥 What did we just make?

 - The circuit has **four connections**.
- Two are **power-supply** related.
 - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.




🔥 Symbolic

🔥 Voltage

A	Q	A	Q
Vss	Vdd	0 V	3.3 V
Vdd	Vss	3.3 V	0 V

🔥 What did we just make?

 - The circuit has **four connections**.
- Two are **power-supply** related.
 - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.



🔥 Symbolic

🔥 Voltage

🔥 Binary

A	Q
Vss	Vdd
Vdd	Vss


A	Q
0 V	3.3 V
3.3 V	0 V

A	Q
0	1
1	0



🔥 What did we just make?

 - The circuit has **four connections**.
- Two are **power-supply** related.
 - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.



🔥 Symbolic

A	Q
Vss	Vdd
Vdd	Vss

🔥 Voltage

A	Q
0 V	3.3 V
3.3 V	0 V

🔥 Binary

A	Q
0	1
1	0




🔥 The CMOS inverter

Logisim design of a CMOS inverter for our next lab.

- You can download Logisim from:

<http://sourceforge.net/projects/circuit/>

 - Install Logisim on your own computer and practice outside of lab hours.



NOT




🔥 The CMOS inverter

Logisim design of a CMOS inverter for our next lab.

- You can download Logisim from:

<http://sourceforge.net/projects/circuit/>

 - Install Logisim on your own computer and practice outside of lab hours.




NOT



🔥 PMOS + NMOS = CMOS

- PMOS is good for making connections to Vdd. |
- NMOS is good for making connections to Vss. ○
 - You can't make a reliable switch (or inverter) with just one type.
 - We either get 1/? or ?/0; we want 1/0.
- So we use a **pair**, one PMOS, one NMOS.
- They are **complementary**.

 

CMOS

Complementary Metal Oxide Semiconductor




Boolean logic in CMOS

- We have a CMOS inverter.
 - Implements “not”
 - In a logic circuit, we call this a **NOT gate**.
- To build a more complex circuit, we need more than just a not gate.

So ... what (else) can we make?



🔥 So ... what (else) can we make?

 


What is this?
How does it work?
NOR

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0



🔥 So ... what (else) can we make?

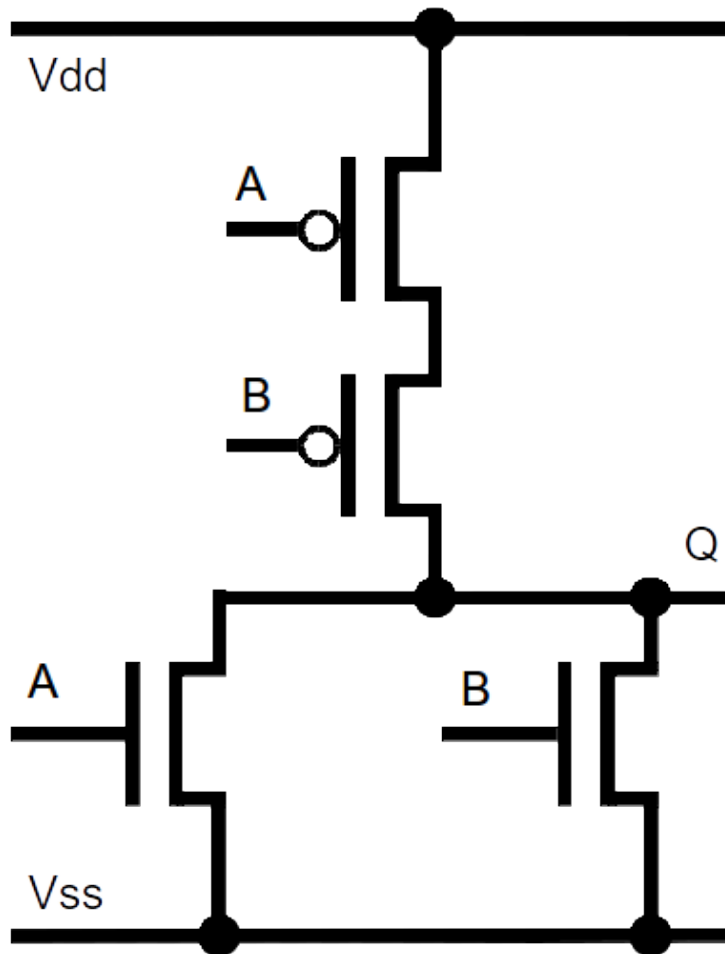


What is this?

How does it work?

Please pause to see whether you can work this out. Carry on only when you've tried.




🔥 So ... what (else) can we make?

 

What is this?
How does it work?




🔥 So ... what (else) can we make?

 


What is this?
How does it work?




NOR (NOT-OR)

 


- This is a NOR gate.

 

NOR (NOT-OR)

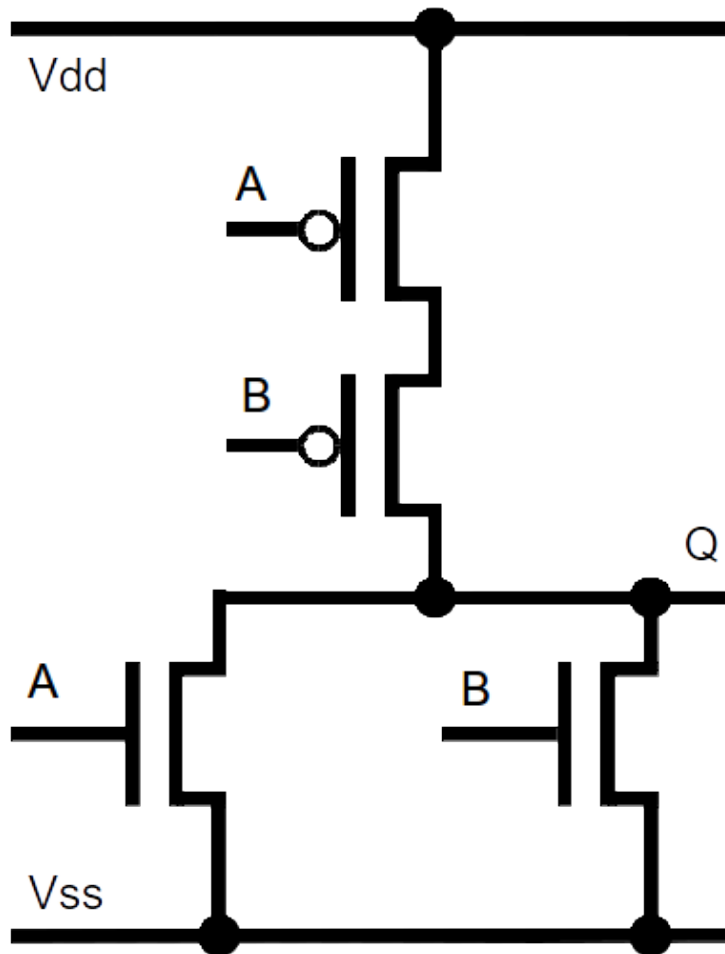


- This is a NOR gate.

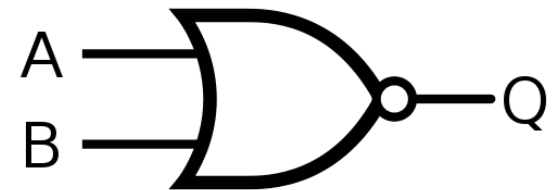


A	B	Q
0	0	
0	1	
1	0	
1	1	



NOR (NOT-OR)

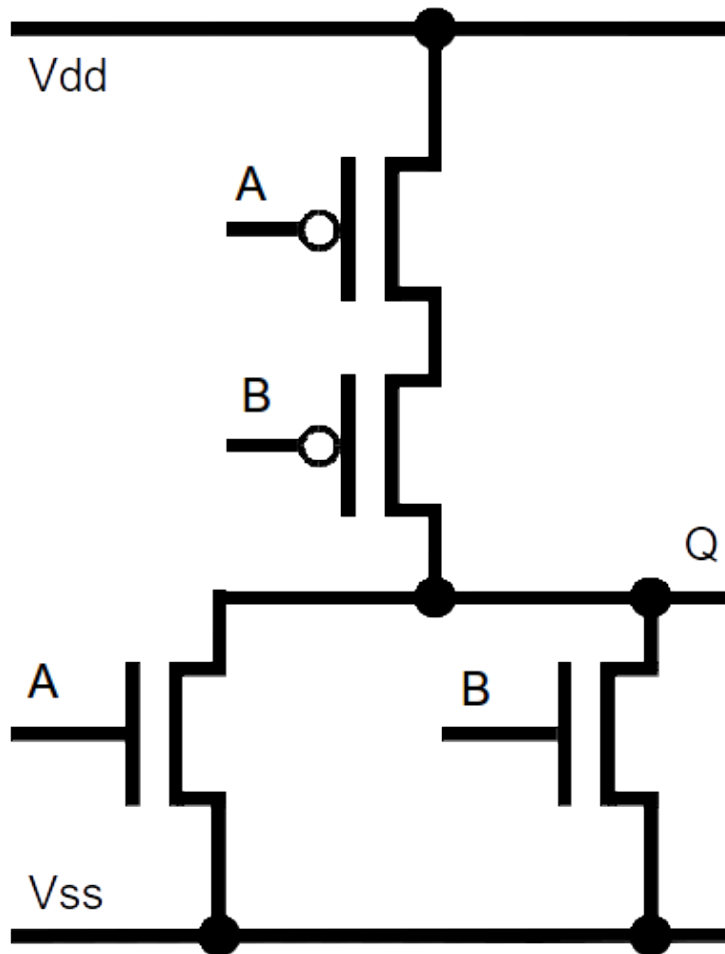


- This is a NOR gate.

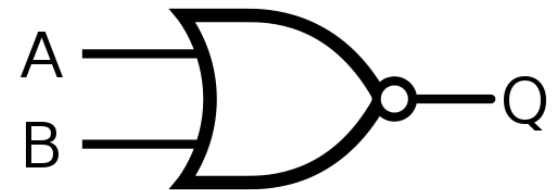

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0




🔥 NAND (NOT-AND)

 

What is this?
How does it work?




🔥 NAND (NOT-AND)

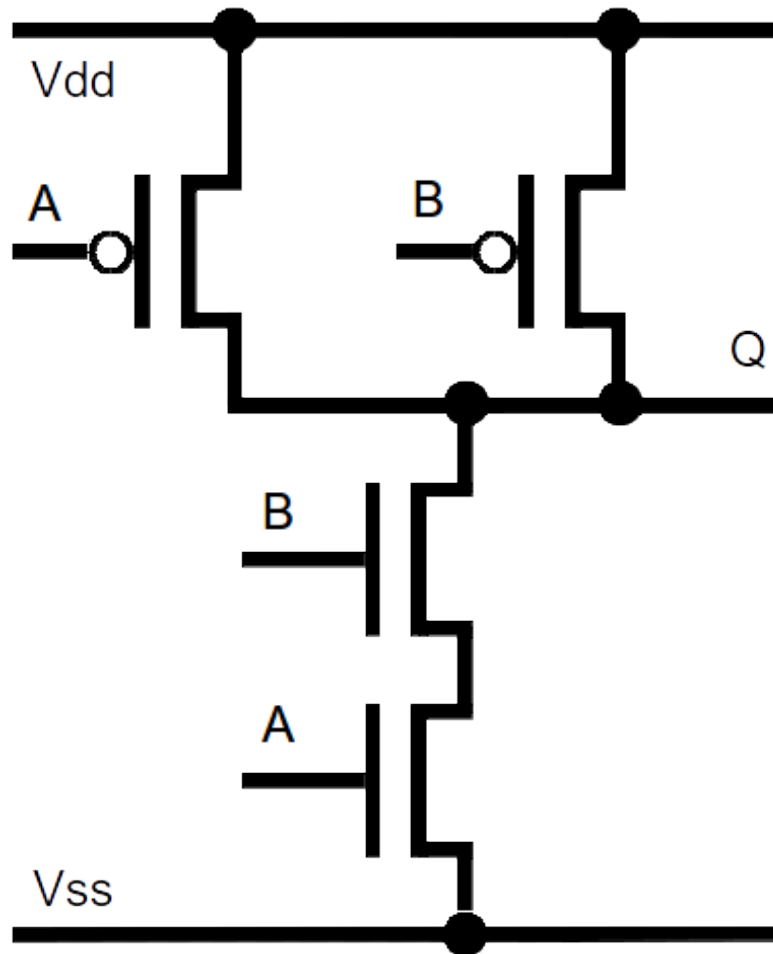

**Can you work out
under which
conditions Q is
connected to Vss?**



🔥 NAND (NOT-AND)

 


- We could also build a NAND gate.



A	B	Q
0	0	
0	1	
1	0	
1	1	



🔥 NAND (NOT-AND)

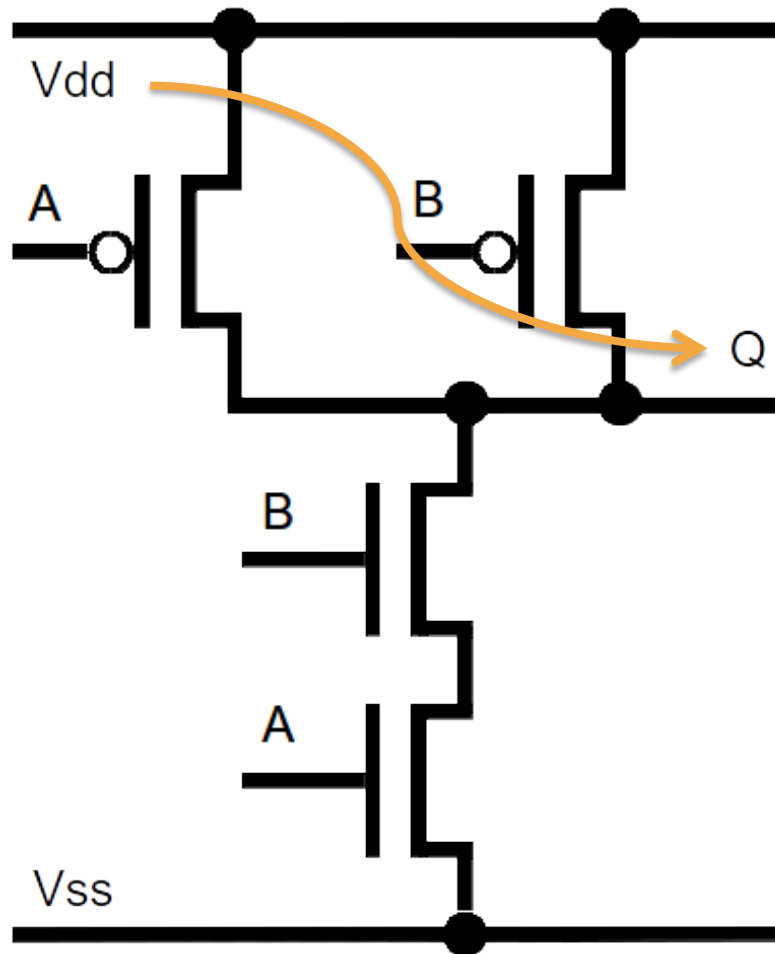


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	



🔥 NAND (NOT-AND)

 


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	



🔥 NAND (NOT-AND)

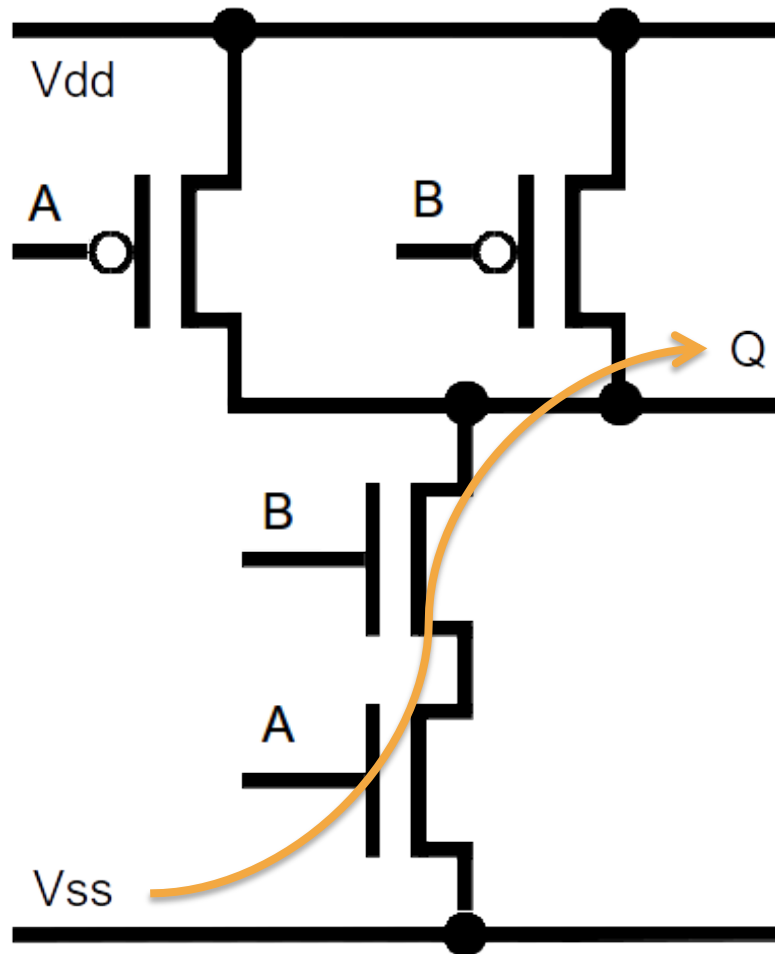


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0



🔥 NAND (NOT-AND)

 


- We could also build a NAND gate.




A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0



NOR and NAND in Logisim

 

NOR

 

NAND

🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

🔥 Diagram



🔥 Boolean algebra

$$Q = \neg(A \wedge A)$$

- Idempotence axiom

🔥 Truth table

A	Q
0	1
1	0

Axioms in Boolean algebra

- Some rules help us avoid evaluating parts, because we can know the answer regardless of the values of the variables.

Rule	Axioms
Identity	$x \wedge 1 \equiv x$
Null	$x \wedge 0 \equiv 0$
Idempotence	$x \wedge x \equiv x$
Inverse	$x \wedge \neg x \equiv 0$

From Lecture 2
Boolean Algebra

- Duality:** Swap 0s and 1s, conjunction and disjunction. Equivalence property is preserved.

🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

🔥 Diagram



🔥 Boolean algebra

$$Q = \neg(A \wedge A)$$

- Idempotence axiom

$$x \wedge x \equiv x$$

$$\neg(\underline{A} \wedge \underline{A}) \equiv \neg(\underline{A}) \equiv \neg \underline{A}$$

🔥 Truth table

A	Q
0	1
1	0

🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

🔥 Diagram



🔥 Boolean algebra

$$Q = \neg(A \wedge A) = \neg A$$

- Idempotence axiom

$$x \wedge x \equiv x$$

$$\neg(\underline{A \wedge A}) \equiv \neg(\underline{A}) \equiv \neg \underline{A}$$

🔥 Truth table

A	Q
0	1
1	0




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

🔥 Diagram

 

$$t0 = \neg(A \wedge B)$$

🔥 Algebra

$$Q = \neg(t0)$$

🔥 Truth table

A	B	t0	Q
0	0		
0	1		
1	0		
1	1		




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

🔥 Diagram

 

$$t0 = \neg(A \wedge B)$$

🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge B)) \\ &= A \wedge B \end{aligned}$$

- Double negation axiom
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

🔥 Truth table

A	B	t0	Q
0	0		
0	1		
1	0		
1	1		




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

🔥 Diagram

 

🔥 Algebra

$$Q = \neg(\neg(A \wedge B)) \\ = A \wedge B$$

- Double negation axiom
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

🔥 Truth table

A	B	t0	Q
0	0	1	
0	1	1	
1	0	1	
1	1	0	




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

🔥 Diagram

 

🔥 Algebra

$$Q = \neg(\neg(A \wedge B))$$
$$= A \wedge B$$

- Double negation axiom
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

🔥 Truth table

A	B	t0	Q
0	0	1	
0	1	1	
1	0	1	
1	1	0	




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

🔥 Diagram

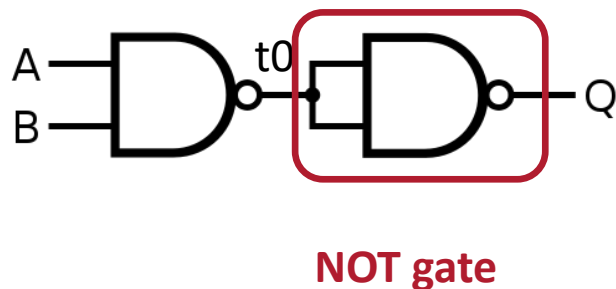

🔥 Algebra

$$Q = \neg(\neg(A \wedge B))$$
$$= A \wedge B$$

- Double negation axiom
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

🔥 Truth table

A	B	t0	Q
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

 

🔥 Algebra

$$Q =$$

🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

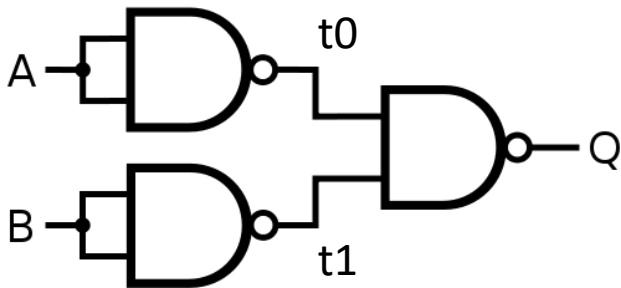

🔥 Algebra

$$Q = \neg(t0 \wedge t1)$$

$$t0 = \neg(A \wedge A)$$

$$t1 = \neg(B \wedge B)$$

🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

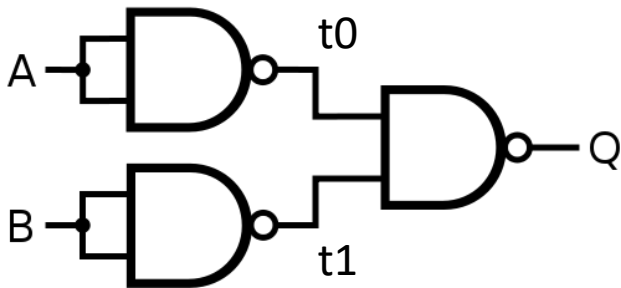

🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

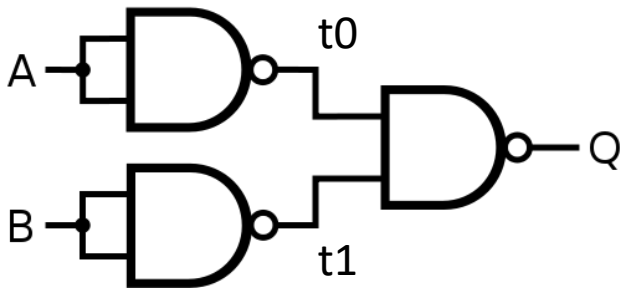

🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

- Idempotence, de Morgan and double negation

🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




🔥 Why NAND?



- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

 

🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

- Idempotence, de Morgan and double negation

🔥 Truth table

A	B	t0	t1	Q
0	0	1	1	
0	1	1	0	
1	0	0	1	
1	1	0	0	




🔥 Why NAND?



- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

🔥 Diagram

 

🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$


- Idempotence, de Morgan and double negation

🔥 Truth table

A	B	t0	t1	Q
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1




🔥 Why NAND?

 

- NAND is an excellent **building block** for other Boolean logic.
- **NAND is functionally complete.**
 - All gates can be expressed with NAND gates arranged in various ways.
- **NOT, AND, OR** as previously shown.
- As well as **NOR**, **XOR**, **XNOR**.
 - **NOR** is also functionally complete.
 - **NOR** structure is slower than NAND.

🔥 Voltages and logic levels

 

- Simplified view so far.
- **Ideal** would be a **right-angled** response.
- Steepness and position of curve depend on transistor **properties**.
- There is also a **delay** between a change in input producing a change in output.
- This delay accounts for the **physical signal propagation time** in silicon.



COMSM1302 NAND Lab 1-3




- NAND boards have either been sent to you or are ready for you to collect.
- The NAND boards are for you to work on your lab sheets during scheduled lab hours or on your own.
- **Please be careful with the NAND boards. They have sharp edges and are sensitive electronic devices.**



Summary

- Switches
 - Mechanical
 - Thermionic
 - Silicon
- Transistors
- CMOS
 - Inverter
 - NAND (functionally complete)
 - Making other gates from NAND
- More about how chips are made:
 - <https://www.youtube.com/watch?v=qm67wbB5Gml>
 - <https://www.youtube.com/watch?v=4FLBtQC0F0c>
 - <https://www.youtube.com/watch?v=i8kxymmjd0M>and this is also quite cool:
 - <https://www.youtube.com/watch?v=Y33cf-lcq-g>

 

The physical layout of a NAND circuit. [Source: By Jamesm76 at English Wikipedia -

Transferred from en.wikipedia to Commons., Public Domain,
<https://commons.wikimedia.org/w/index.php?curid=294462>]



In this lecture

Foundations

- Data representation, logic, Boolean algebra.

Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

Modules

- Memory, simple controllers, FSMs, processors and execution.

Programming

- Machine code, assembly, high-level languages, compilers.

Wrap-up

- Operating systems, energy aware computing.



In the next lecture

Foundations

- Data representation, logic, Boolean algebra.

Building blocks

- Transistors, transistor based logic, **simple devices**, storage.

Modules

- Memory, simple controllers, FSMs, processors and execution.

Programming

- Machine code, assembly, high-level languages, compilers.

Wrap-up

- Operating systems, energy aware computing.

